
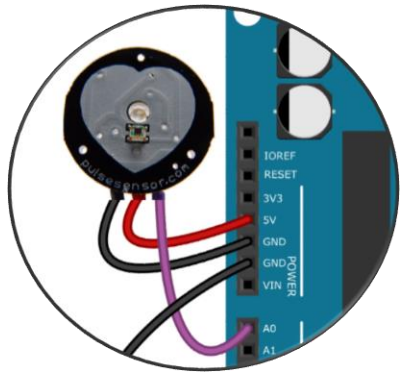


Make Your Own Pulse Sensor – Assembly Instructions


Step 1: Connect the Sensor

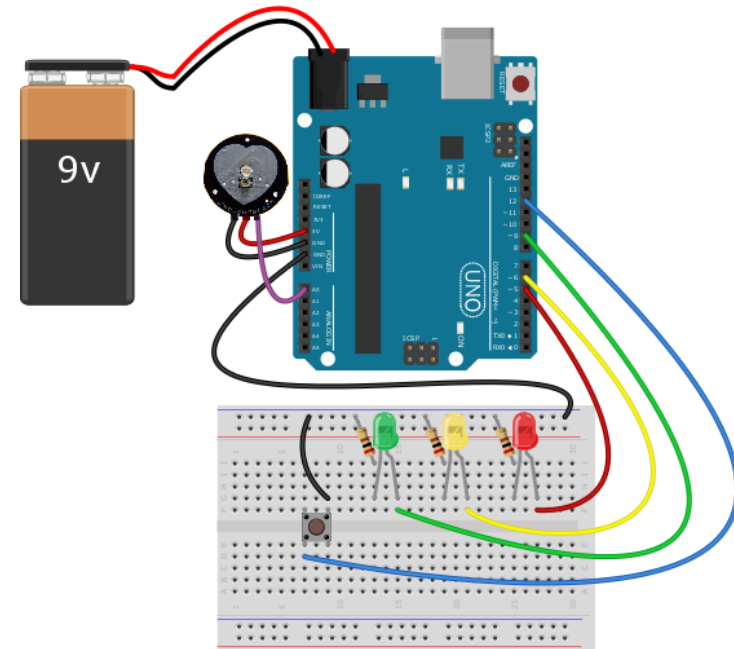

- With the pulse sensor facing you so you see the heart, connect the left most wire (-ve) to the pin marked GND on the UNO (see picture to the left)
- Next connect the middle wire (+ve) to the pin labelled 5V
- Connect the right most wire (signal) to the pin labelled A0
- Connect the 9V battery to the power connector on the corner of the UNO
- To test, lightly hold the sensor to your thumb, being careful not to touch the components on the back. The heart graphic should be against your thumb. When positioned correctly the light on the UNO labelled L will pulse in time with your heart beat




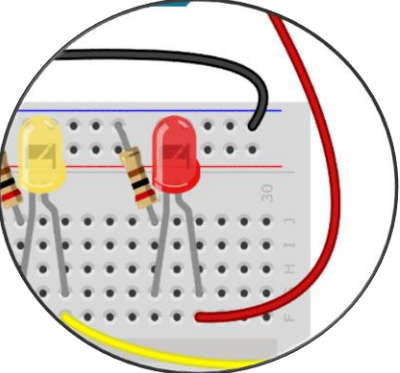Step 2: Connect One Light Emitting Diode (LED)



- Before continuing, disconnect the battery
- Install a red LED and resistor as shown. Use a 220 ohm resistor (the one with two pink stripes)
- Using a jumper wire connect the positive side of the LED to pin 5 on the UNO
- Connect the blue ground rail to the second GND pin on the UNO using a jumper wire
- Now if you connect the battery and place the sensor against your thumb the red LED should blink in time with your pulse

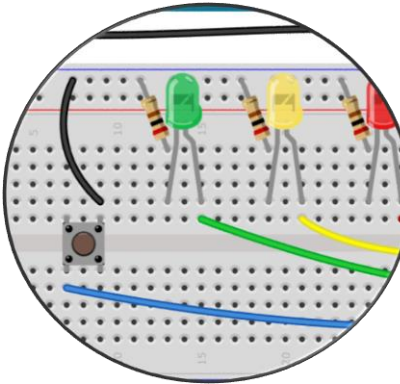Step 3: Connect the Remaining LEDs and Button



- Repeat Step 2 for the remaining two LEDs and resistors. Also connect the button. Refer to the image on the right for the corresponding microcontroller connections
- Once complete, when the battery is connected your system will change how it displays your pulse depending on how many times the button has been pushed

